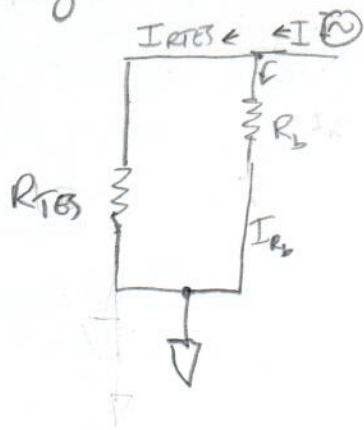


Voltage Bias



Page 1 (17)

Thermin $I_{TES} + I_{R_b}$

$$\frac{1}{R_{tot}} = \frac{1}{R_{TES}} + \frac{1}{R_b}$$

Voltage Bias for TES

$$R_{total} = \frac{R_b R_{TES}}{R_{TES} + R_b}$$

$$V_{total} = \frac{I R_b R_{TES}}{R_{TES} + R_b}$$

If $R_b \ll R_{TES}$

$$V_{total} = \frac{I R_b R_{TES}}{R_{TES}} \Rightarrow I R_b$$

V_{bias} requirement is set by bolometer properties
 $\Rightarrow P_{optical} \rightsquigarrow P_{electrical}$

SPT-3G example $R_{TES} = 1 \Omega$ bolometer

$P_{optical} \sim 7 \mu W$

$P_{electrical} \sim 7 \mu W \rightarrow V_{bias} \approx 3 \mu V$

$\Rightarrow I_{R_{TES}} \sim 3 \mu A$

Assuming R_{TES} fluctuates by 1% rms
 in reaction to sky signal (this is big)
 \rightarrow need to be able to read out 30 nA signal

16 bit ADC $\frac{1V}{2^{16}} \sim 15 \mu V$ resolution

\rightarrow need amplification w/o introducing noise

The SQUID

- superconducting quantum interference device
- extremely sensitive to external magnetic flux
- can detect $\Delta\phi \sim 10^{-4} \phi_0 \sqrt{\text{Hz}}$

$\phi_0 = \frac{h}{2e} \rightarrow$ flux quantum
 $\sim 2 \times 10^{-15}$ Webers or

$1 G = 10^{-4} T$



$1 T = 1 W/m^2$

Earth magnetic field $\sim 10^{-4} W/m^2$

- low noise
- high forward gain
- large operational bandwidth

But also drawbacks
 → dynamic range
 → cryogenic

Building block of a SQUID 1) is the Josephson junction

2) flux quantization in a superconducting ring

$2\pi n = \oint \nabla\phi dl \Rightarrow \Phi$

magnetic flux through contour

The Josephson Junction

$\psi_0 \Rightarrow$ Cooper pair density

$\phi_0 \Rightarrow$ center of mass motion of Cooper pairs



Cooper pairs can tunnel through the barrier

2 equations to describe behavior

Cooper pair = pairs of charge carriers in superconductor ee

1) $I_J = I_c \sin \delta$

current phase relation

$I_c =$ critical current \rightarrow maximum supercurrent

$\delta = \phi_1 - \phi_2 =$ phase difference between the wavefunctions of S1 & S2

$I =$ supercurrent across the junction

$\hbar = \frac{h}{2\pi}$

EQN #1 comes from \Rightarrow phase gradient eqn
must gradient across the

- \rightarrow calculate current as a function of δ
- \rightarrow rewriting as a Fourier series
- \rightarrow considering only 1st sine term

Voltage-phase relation 2) $\hbar \frac{d\delta}{dt} = \frac{2eU}{\hbar} = \frac{2\pi}{\Phi_0} U$ where $\Phi_0 = \frac{h}{2e} =$ magnetic flux quantum

ie if the phase across the junction varies, a potential develops

RCJ Model

More realistic model

\rightarrow Stray capacitance due to junction geometry



resistively & capacitively shunted junction

\rightarrow resistive shunt due to non-zero quasiparticles (single electrons) & purposeful to prevent hysteresis

$$\Rightarrow I = I_J + I_R + I_C$$

$$= I_c \sin \delta + \frac{U}{R} + C \frac{dU}{dt} \quad \text{insert eqn \#2}$$

$$I - I_c \sin \delta = \frac{\hbar}{2eR} \dot{\delta} + \frac{C\hbar}{2e} \ddot{\delta}$$

Note \rightarrow ignore noise

Analogous to damped harmonic oscillator w/ non-linear force term


\Rightarrow Solution $U = -I\delta - I_c \cos \delta$

Voltage as a function of phase difference


- \rightarrow washboard potential
- \rightarrow bias current tilts it to allow voltage to develop



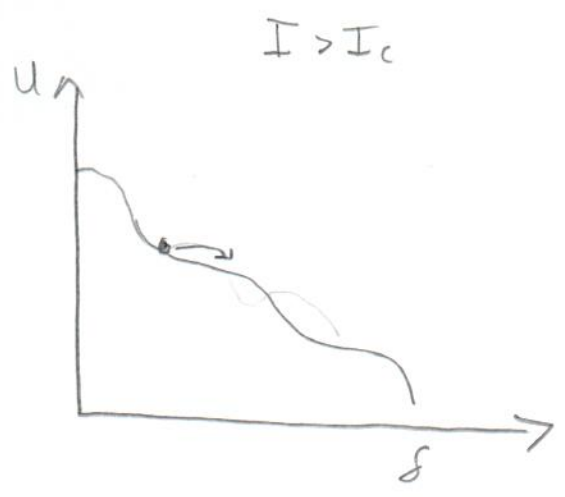$\langle \delta(t) \rangle \Rightarrow \langle U(t) \rangle = \phi$



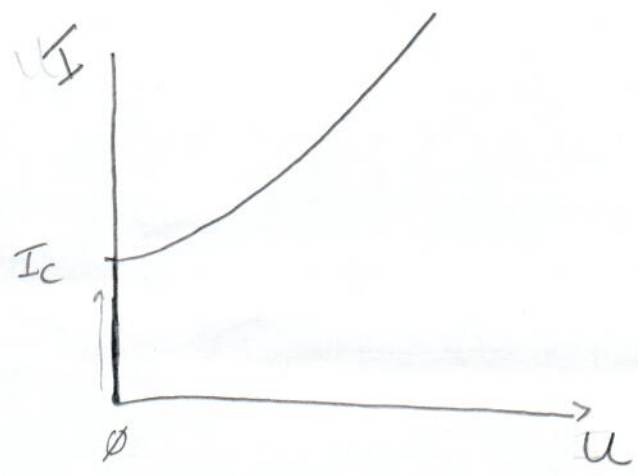
$\langle \delta(t) \rangle \Rightarrow \langle U(t) \rangle \neq \phi$




this leads to the following IV curve for a SQUID

The DC SQUID

2 Josephson junctions in parallel

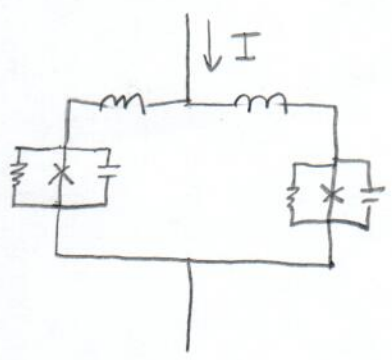

\Rightarrow simplify

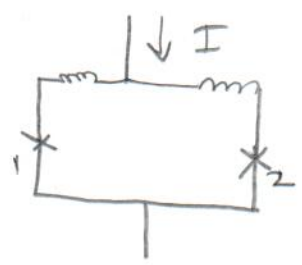


superconducting ring biased w/ current I

Max ^{super} current in the loop = $I_{c1} + I_{c2}$
 Bias w/ $I > I_c$

Read V as a function applied Φ
 Φ modulates $I_c \rightarrow$ which changes U

when I_c is max V is min

I_c is min V is max

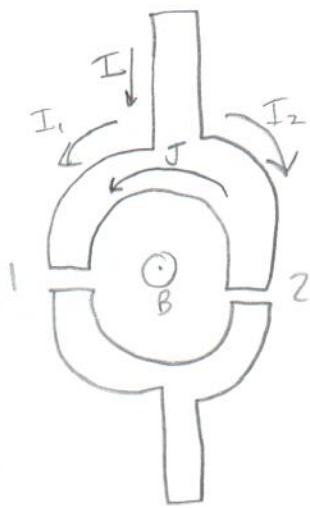

Flux wants to be integer multiple Φ_0

current through each junction is

$$I_1 = \frac{I}{2} + J$$

$$I_2 = \frac{I}{2} - J$$

⇒ Back to the RCST model

$$\frac{I}{2} \pm J = I_c \sin \delta + \frac{\hbar}{2el} \dot{\delta} + \frac{C\hbar}{2e} \ddot{\delta}$$

Phase differences across the junctions are related to the total flux

→ 2 components

N.B. this coupling is dictated by SQUID layout

- 1) external magnetic field
- 2) circulating current


$$\delta_2 - \delta_1 = \frac{2\pi}{\Phi_0} (\Phi_A + LJ)$$


In the static case

can solve for $I_c(\Phi_A)$

$$I_{c_{tot}} = 2I_c \left| \cos\left(\pi \frac{\Phi_A}{\Phi_0}\right) \right|$$


(simplified assumptions)

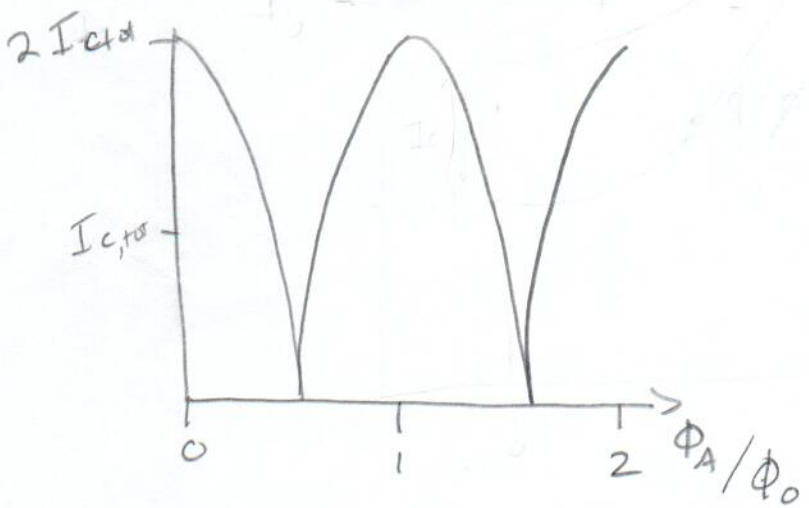

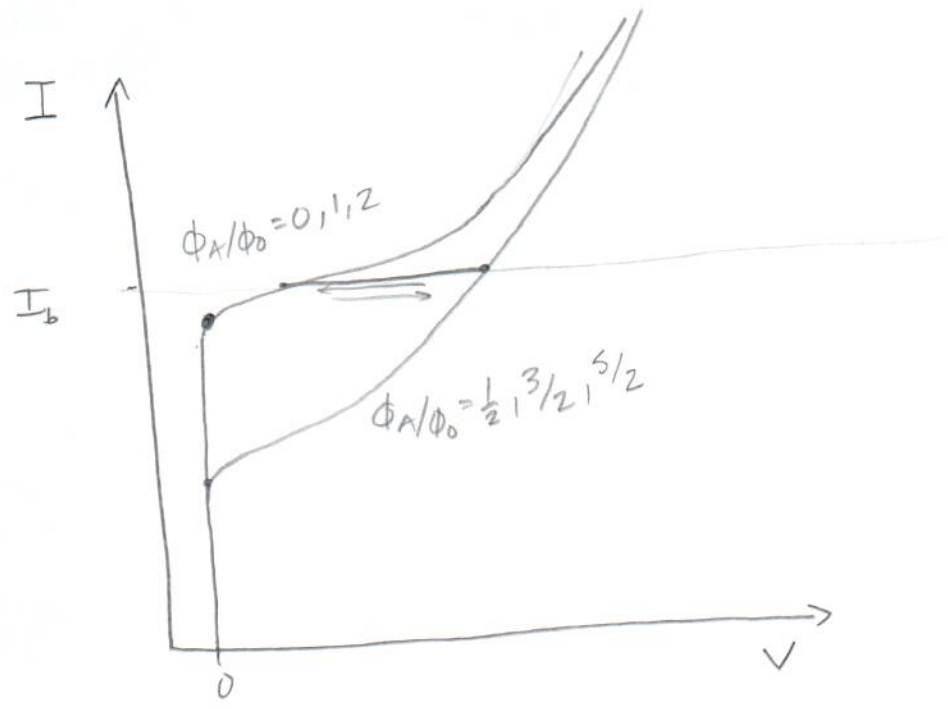

Must solve current equations for non-static case to allow voltage to develop

⇓

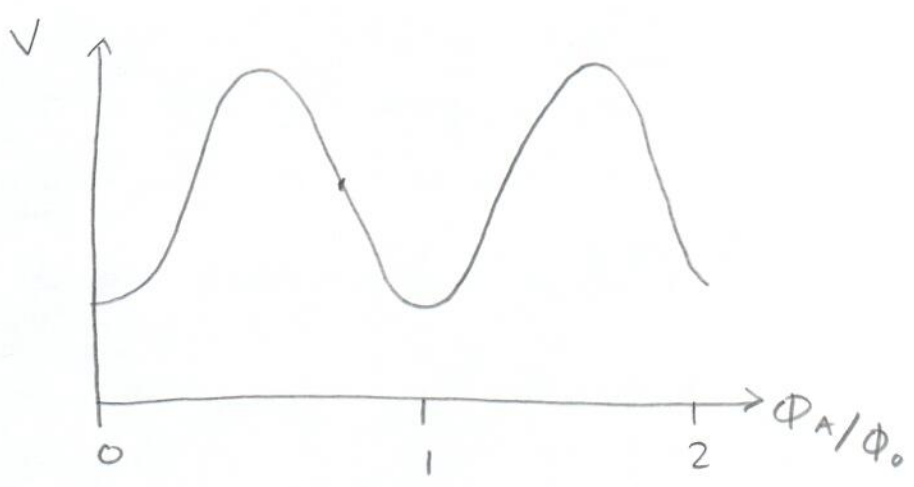


→ Magnetic flux coupled via inductor input coil

Can maximize ΔV for $\Delta\Phi_A$

→ find $\frac{\partial V}{\partial \Phi_A}$ is max

Can use V_{pp} as a proxy

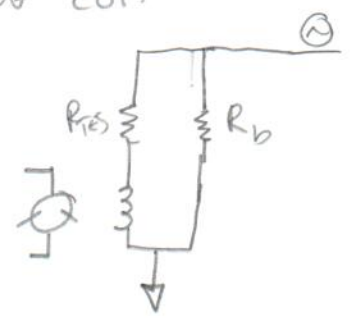

Transimpedance → quoted in Ω

$$Z_{SQ} = M \frac{\partial V}{\partial \Phi}$$


⇒ output voltage given input current

The RF SQUID

7

Single junction

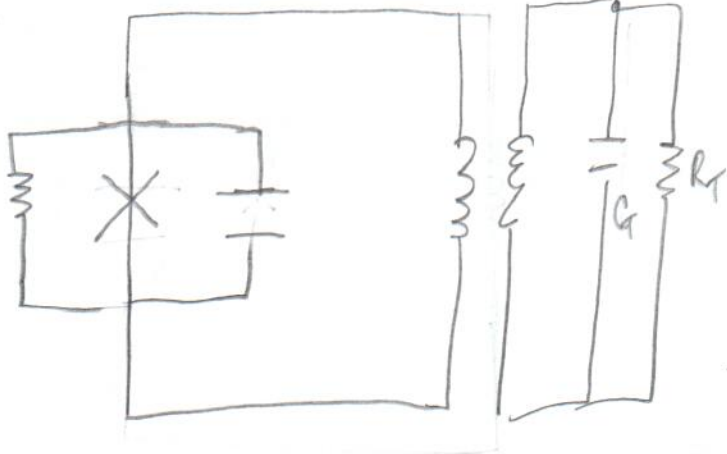
Inductively coupled to a resonant circuit which is driven at its resonant frequency



Standard

loop has self

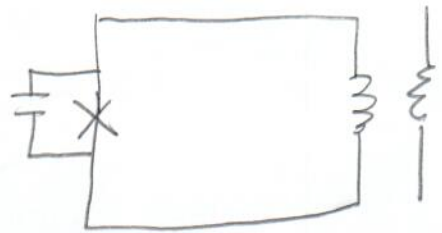inductance, current that tunnels across junction also drives flux in the loop



Dissipationless


- higher noise than DC SQUID
- require AC readout
- simpler fab

Flux coupling into the SQUID

→ self inductance depends on mean flux

→ change resonance of the tank

Simple Readout w/ DC SQUID

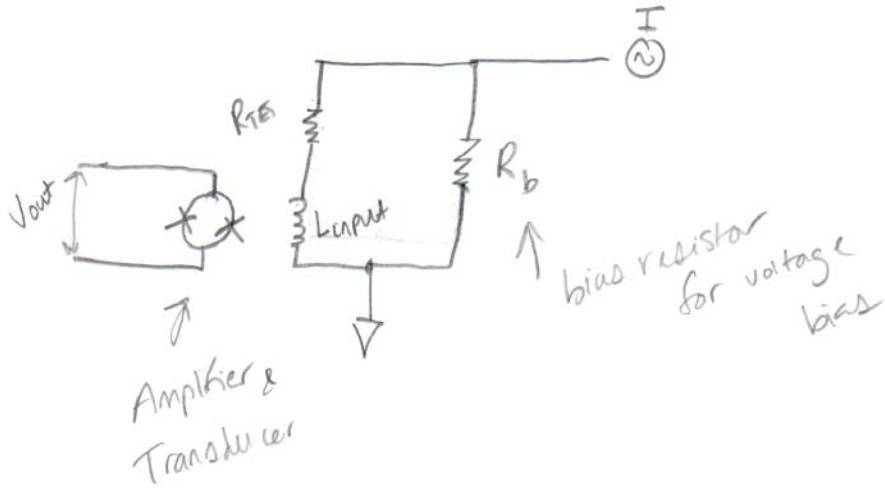

But really, we use arrays of SQUIDS
 → can yield few mV of signal

Series SQUID array

→ voltages increase w/ N

→ noise adds quadrature

$$\sigma_{SSA}^2 = N \sigma_s^2 \Rightarrow \sigma_{SSA} = \sqrt{N} \sigma_s$$

→ win in S/N by \sqrt{N}

caveat for SSA

→ increased sensitivity to trapped flux & external magnetic fields

→ don't want gradients across the SSA so that they add coherently

Multiplexing required

- 1) Time division multiplexing
 - 2) Frequency division multiplexing
 - 3) μ -multiplexing
 - 4) MKIDs
- } DC SQUIDS
 - RF SQUIDS

First 3 all use SQUIDS, but in different ways.

Will talk about #4 later (also Erik Shirokoff)


TESs require subkelvin operation \Rightarrow limited power dissipation
 \Rightarrow 2 wires per detector not possible as focal plane sizes increase (& we are there now)
 or cryocooler

TDM

\Rightarrow TES is DC biased

First stage SQUID inductively coupled to each TES
 single column

Uses a common bias line

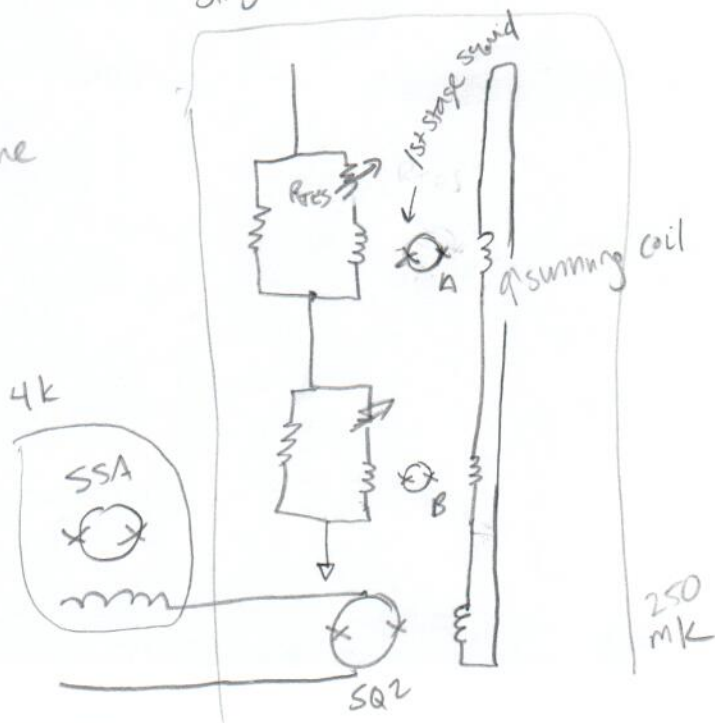

SQUIDS are biased sequentially
 \rightarrow A, then B
 the summing coils couples into 2nd stage SQUID
 \rightarrow couples into an SSA for amplification

Uses flux lock loop in multiple stages

→ feeds back on output of SSA to keep it constant

Use → FE

Updated TDM architecture for Adv. Act (eliminates SAR)
→ uses Flux Activated switches for row select (Array of Josephson junctions)

Example of switching

rate → row rate = 560 kHz for ACT

full array = 15.2 kHz
(every 65 μs)

Limitation → limited sampling rate

→ high-f noise is aliased into signal band

⇒ results in increased noise

→ can be mitigated by bandwidth limiting signals from TES above Nyquist

Adv. Act 64 rows x 32 columns

↓
Nyquist
inductor

Frequency Division Multiplexing

→ This is the one you'll use in the lab this afternoon (11)

ACBIAS

TES is AC biased

$$I(t) = A \cos \omega_c t$$

current through TES from voltage bias

optical signal $\rightarrow I_y = a_y \cos \omega_y t$

Define the AM modulated waveform $I_m = A \cos \omega_c t (1 + a_y \cos \omega_y t)$

$$= A \cos \omega_c t + a_y A \cos \omega_c t \cos \omega_y t$$

\Rightarrow trig identity

$$= A \cos \omega_c t + \frac{a_y A}{2} [\cos(\omega_c - \omega_y)t + \cos(\omega_c + \omega_y)t]$$

original carrier


sky signal @ $\omega_c \pm \omega_y$

\rightarrow the sidebands

Can multiply by unmodulated reference @ original bias frequency to demodulate down to base band & measure $\int a_y \cos \omega_y t dt$


Amplitude Modulation

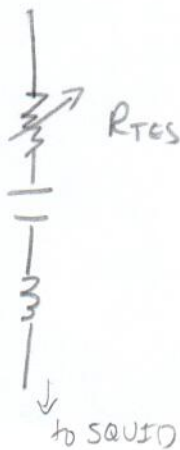In FDM \rightarrow each TES in a module is assigned a unique resonant frequency



$$f_0 = \frac{1}{2\pi\sqrt{LC}}$$

$$\Delta f = \frac{R}{2\pi L}$$

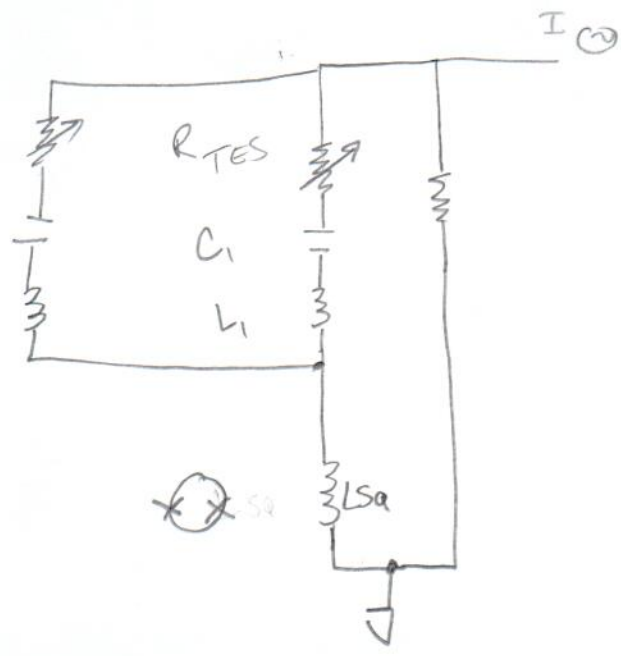

Make a parallel network that is summed together and then inductively coupled into a DC SQUID

AC Biased TES
DC SQUID → for amplification

Feedback

old generation → combo of FLL & injected nuller

→ New generation

- digital waveform w/ active feedback (subtract carriers & sidebands)
- nuller becomes the signal you readout

Limitations

How many channels can pack into a given bandwidth w/ acceptable crosstalk

Macroscopic components

$$\Delta f_{elec} > 5.8 \Delta f_{thermal}$$

Electrical circuit bandwidth must be $5.8 \times$ TES bandwidth


→ or TES could oscillate at frequencies & circuit couldn't respond

dissipationless rf SQUID used to provide gain between TES & HEMT

→ self inductance depends on the flux

→ couple to microwave resonator (Gitz frequencies)

→ each w/ unique resonant frequency

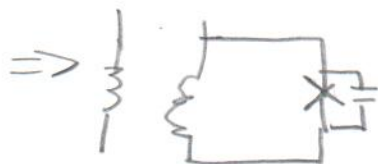

TES is DC biased w/ parallel shunt resistor

→ multiple TESs share single pair of bias wires

Modulations in TES resistance modulate

flux through SQUID

→ couples to the resonator & modulates its resonant frequency

Measure the shifting resonance w/

a fixed tone → single coax

- SQUID noise
- HEMT noise
- TES noise

Mustang 2 → 215 elements

SO

NB: HEMT = high electron mobility transistor

→ cryogenic amplifier