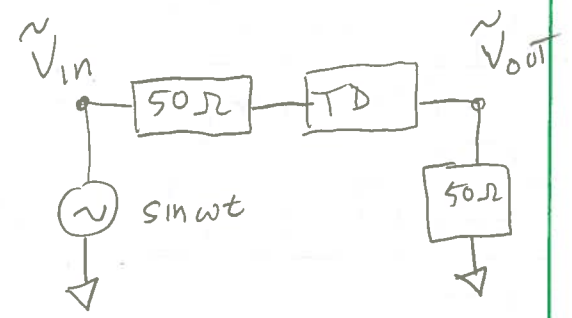


IN FREQUENCY SPACE, ANY SIGNAL CAN BE REPRESENTED AS $I \cdot \sin(\omega t) + Q \cdot \cos(\omega t)$

FOR LINEAR CIRCUITS, WE CAN CONSIDER EACH ω INDEPENDENTLY.


THE CIRCUITS WE'LL BE DISCUSSING LOOK LIKE THIS:




$$S_{21} = \underbrace{\text{Amplitude of sin comp. at P2.}}_{\text{"I"}} + i \times \underbrace{\text{Amplitude of cos. comp.}}_{\text{"Q"}}$$

S_{11} = THE SAME, BUT W.R.T. POWER REFLECTED FROM THE DEVICE BACK TO P1


x 13

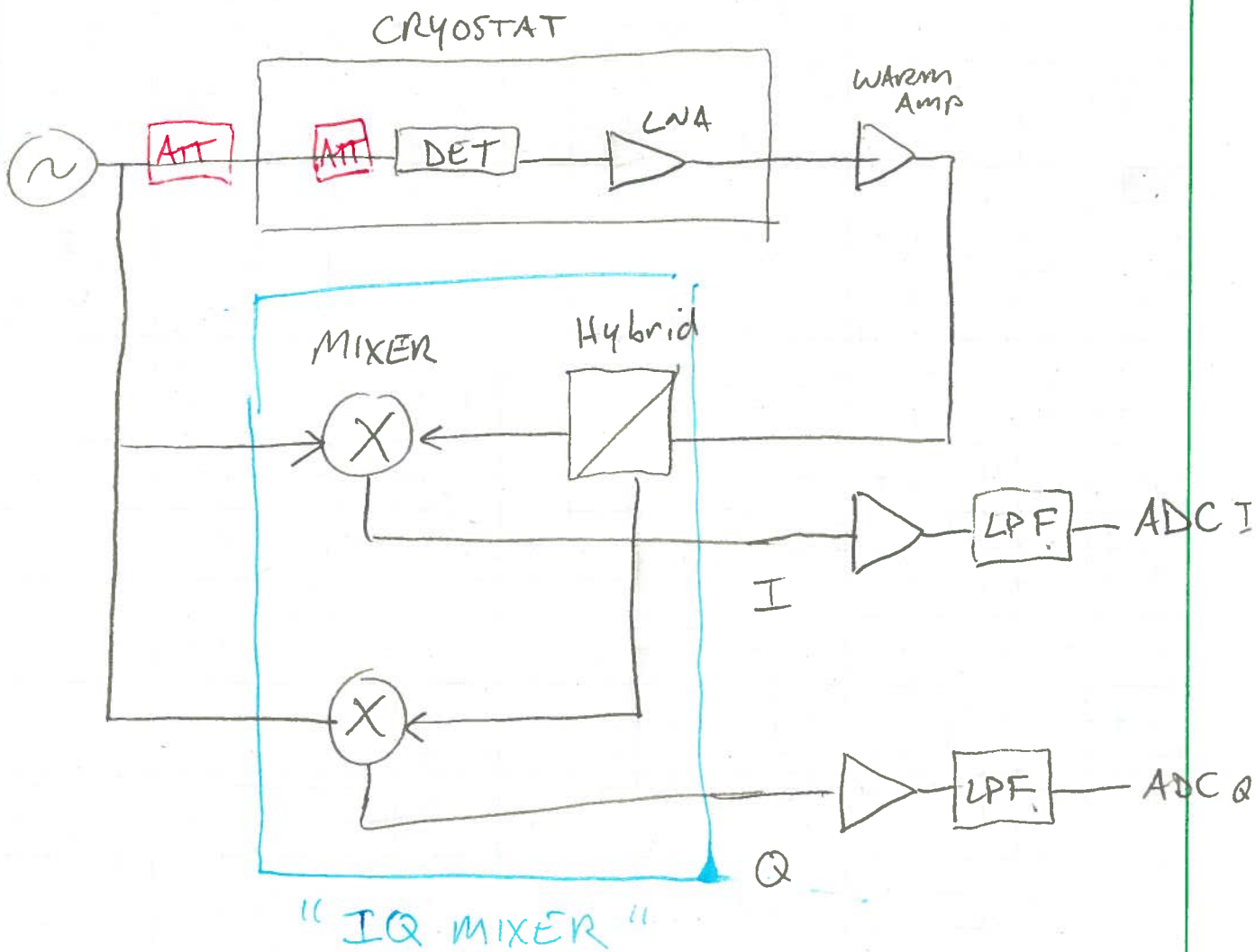

RESONATOR CIRCUIT :

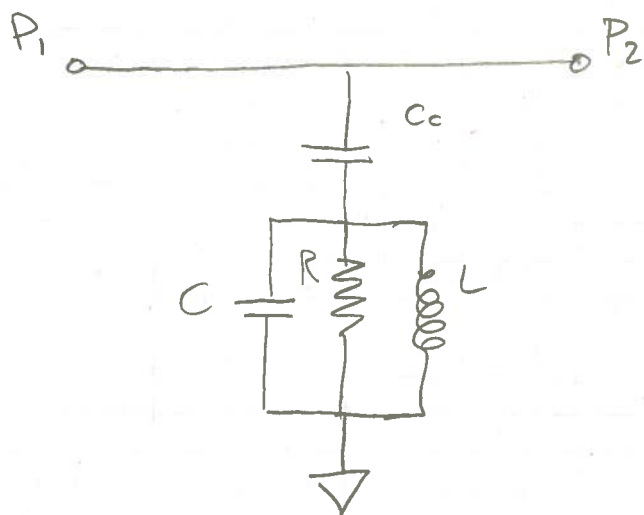
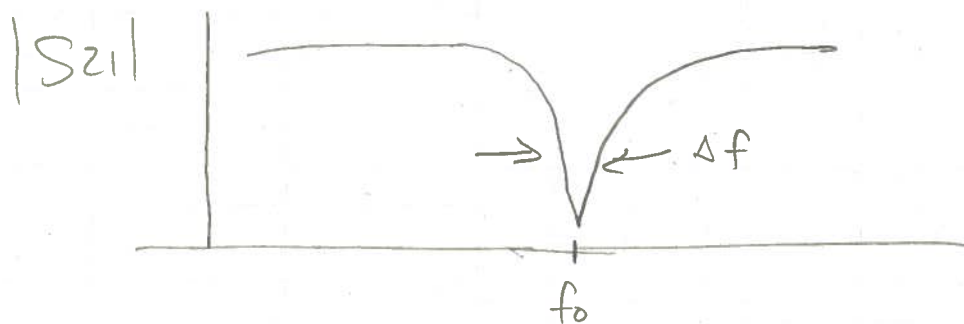
$$\omega_0 = 2\pi f_0 = \frac{1}{\sqrt{LC}}$$



$Q_r \equiv \frac{f_0}{\Delta f} =$ fraction of power lost per cycle when the resonator is momentarily excited.

THIS COMES FROM TWO MECHANISMS:

1) Coupling Q : let $R \rightarrow 0$, find power lost to the feed line.

\rightarrow algebra $\rightarrow Q_c = \frac{ZC}{\omega_0 Z_0 C_c^2}$

2) "internal Q": let $C_c \rightarrow 0$, POWER
LOST TO THE RESISTOR GIVES:

$$Q_i = \omega_0 R C$$

WHAT IS R ?

- Q.P. RESISTANCE
 - SURFACE + DIELECTRIC LOSSES.
 - RADIATIVE LOSSES
 - E&M COUPLING TO THE BOX
- etc.


SOME PEOPLE BREAK THIS INTO $Q_i + Q_{LOSS}$
OR SIMILAR.

TOGETHER THESE DETERMINE THE TOTAL Q :


$$Q_R^{-1} = Q_C^{-1} + Q_i^{-1} + \dots$$

WHAT DOES THIS LOOK LIKE IN PRACTICE?

α^4

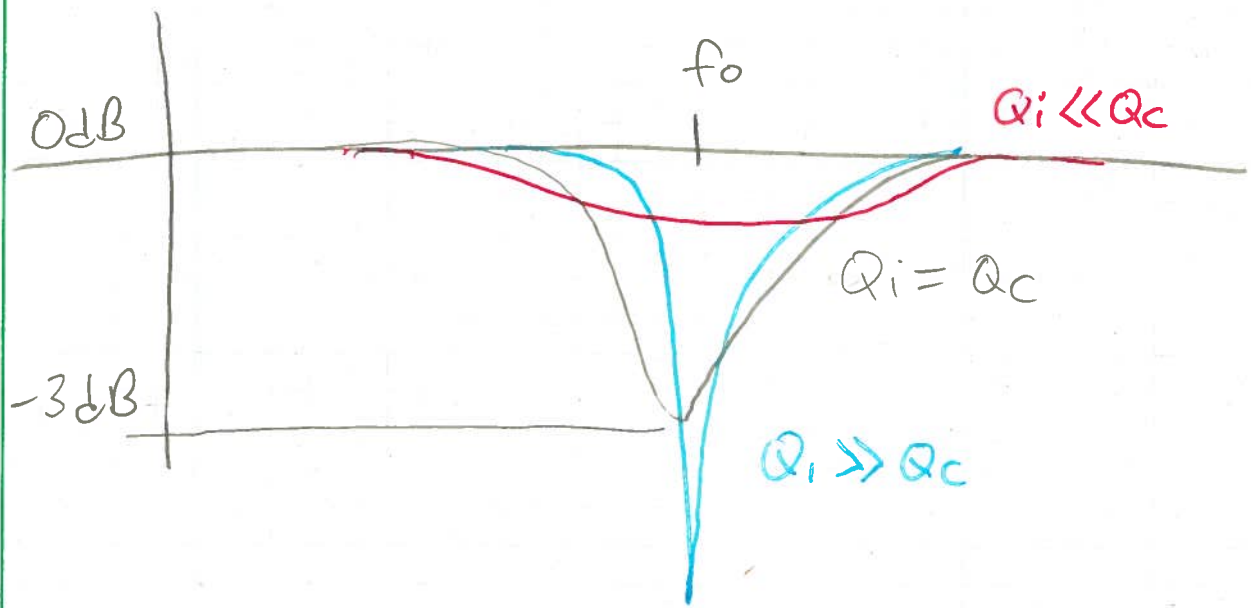

ABOVE PLOT FOR A FIXED Q_c
IN IQ SPACE:

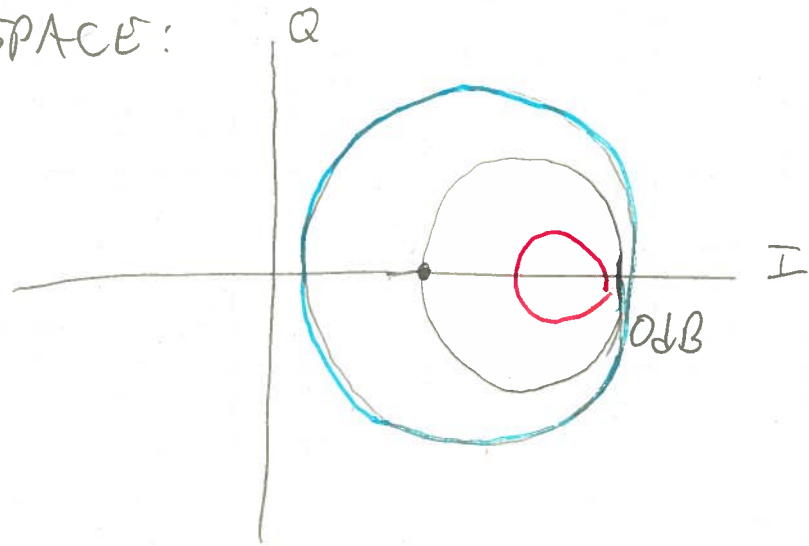

FUNCTIONAL FORM IS APPROX:

$$S_{21} = 1 - \frac{Q_r}{Q_c} \left[\frac{1}{1 + z_j Q_i x} \right]$$

$$x \equiv \frac{\omega - \omega_0}{\omega_0}$$

$$j \equiv \sqrt{-1}$$

- COMPLICATIONS:
- CABLE DELAY
 - NON-MATCHED IMPEDANCES
 - AMPLITUDE, OFFSETS, Freq. dep gain.

MORE GENERAL:

$$Q_c \rightarrow \tilde{Q}_c \equiv Q_c^R + j Q_c^I$$

$$Q_c = |\tilde{Q}_c|$$

(Gao, etc use $Q_c e^{j\phi_0}$ notation)

TO FIT CABLE DELAY ALSO, CAN ADD


$a e^{-j\omega\tau}$ multiplier to whole thing

↑ normalization ↑ cable delay

α56

WHAT HAPPENS WHEN WE SHINE LIGHT ON THIS DEVICE?

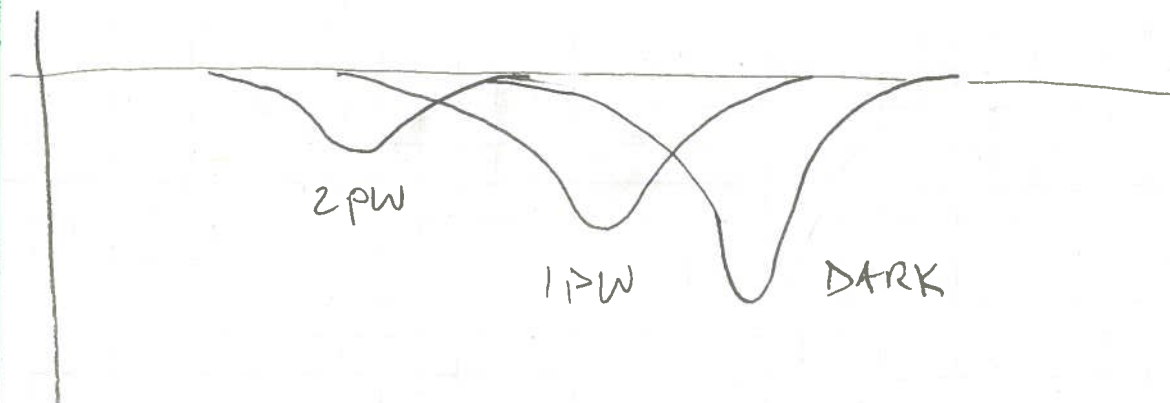L_k and R both change linearly in response to small amounts of optical power.




RESONATOR MOVES TO THE LEFT AND DEPTH DECREASES. (Q_i goes down.)

IN MOST CASES, THE FREQUENCY SIGNAL IS MORE SENSITIVE.

WE WANT TO RECORD $\frac{\Delta f}{f_0}$ VS. time.


So- How DO WE ACTUALLY TAKE DATA?

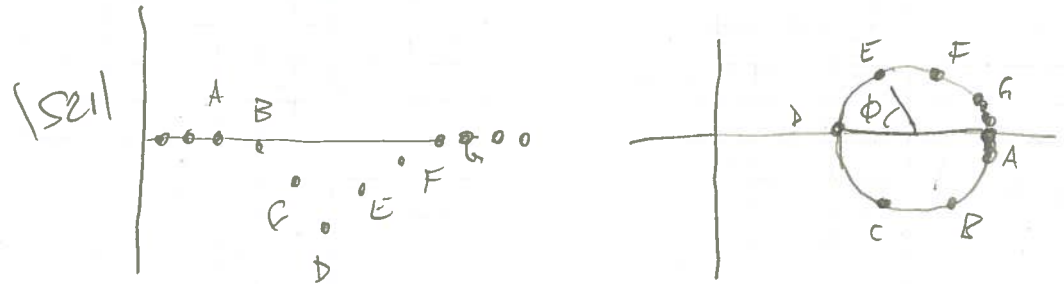1- DO A SWEEP TO FIND f_0 , $\phi(\Delta f)$




NOTE THE POINTS GET FARTHER APART IN $|\Delta I^2 + \Delta Q^2|$.

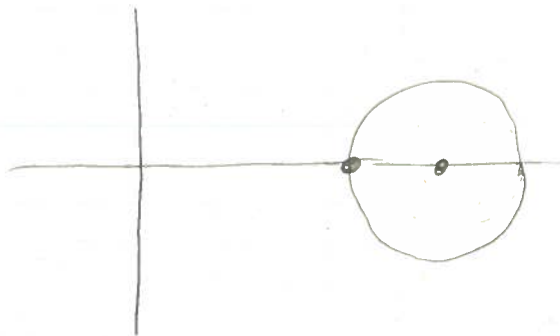2- PLACE A TONE AT f_0 , record $I, Q(t)$
 $\rightarrow \phi(t)$.



WE KNOW $\phi(f - f_0)$ FROM SWEEP.

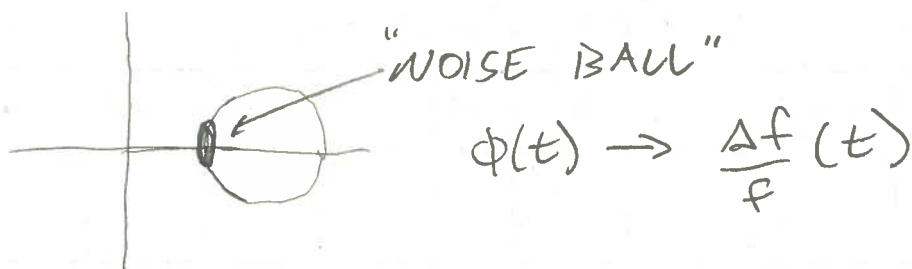NOW $f = \text{fixed}$, f_0 CHANGES WITH POWER ON THE KID.



CONSIDERATIONS:


1. BIFURCATION.

KINETIC INDUCTANCE IS NON-LINEAR TO 1ST ORDER.

$$L_k(I) = L_k(0) \left[1 + \frac{I^2}{I_*^2} \right]$$

SINCE THE CURRENT IN THE RESONATOR IS A FUNCTION OF $f - f_0$, THIS MAKES

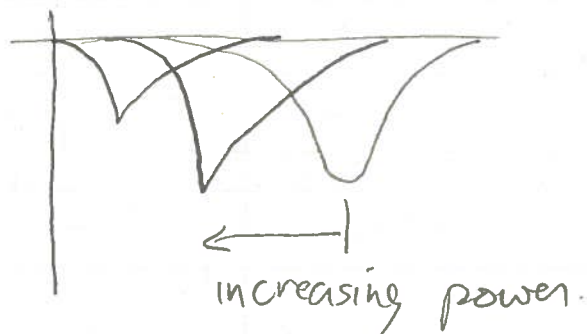$S_{21}(f)$ complicated and power dependent.



EVENTUALLY, $S_{21}(f)$ HAS TWO SOLUTIONS

I_* SCALES WITH: V_L, T_c, N_0